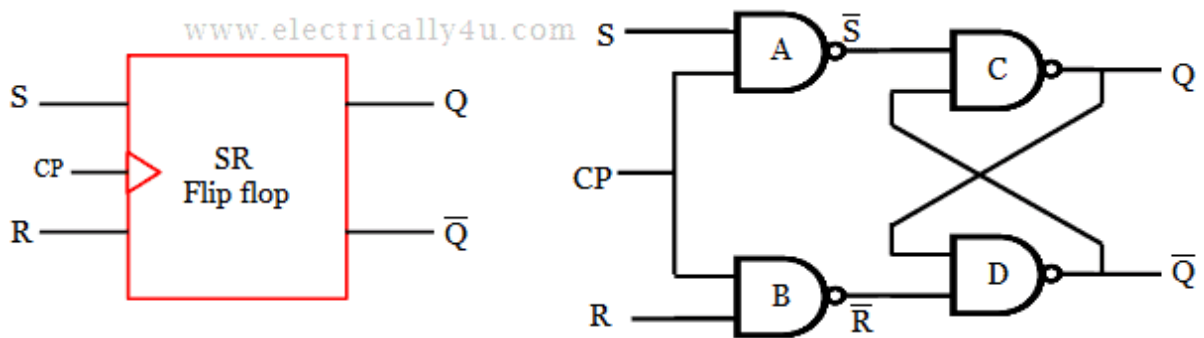


SR FLIP FLOP

It is a Flip Flop with two inputs, one is S and other is R. S here stands for Set and R here stands for Reset. Set basically indicates set the flip flop which means output 1 and reset indicates resetting the flip flop which means output 0. Here clock pulse is supplied to operate this flip flop, hence it is clocked flip flop.



RTL CODE:

```
module tla(input clk,input s,input r,output reg q,output reg qb);  
  always @(posedge clk) begin  
    case({s,r})  
      2'b00: q<=q;  
      2'b01: q<=0;  
      2'b10: q<=1;  
      2'b11: q<=1'bz;  
    endcase  
  end  
  assign qb=~q;
```

```
endmodule
```

TEST BENCH:

```
module test;
```

```
    reg clk;
```

```
    reg s;
```

```
    reg r;
```

```
    wire q,qb;
```

```
    tla t1(clk,s,r,q,qb);
```

```
    initial begin
```

```
        clk=0;
```

```
        forever #10 clk = ~clk;
```

```
    end
```

```
    initial begin
```

```
        $dumpfile("dump.vcd");
```

```
        $dumpvars(1);
```

```
    end
```

```
    initial begin
```

```
        s= 1; r= 0;
```

```
        #10 s= 0; r= 1;
```

```
        #10 s= 0; r= 0;
```

```
        #10 s= 1; r= 1;
```


```
    end
```

```
    initial begin
```

```
        #60 $finish();
```

```
    end
```

```
endmodule
```

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.