 


JK FLIP FLOP

[Flip-flops](#) are fundamental building blocks of sequential circuits. A flip flop can store one bit of data. Hence, it is known as a memory cell. Since they work on the application of a clock signal, they come under the category of synchronous circuits.

The J-K flip-flop is the most versatile of the basic flip flops. The JK flip flop is a gated SR flip-flop with the addition of a clock input circuitry that prevents the illegal or invalid output condition that can occur when both inputs S and R are equal to logic 1. Due to this additional clocked input, a JK flip-flop has four possible input combinations, “logic 1”, “logic 0”, “no change” and “toggle”.



RTL CODE:

```
module tlsa(input clk,input rst,input j,input k,output reg q,output reg qb);  
    always@(posedge clk)begin  
  
        if(rst) begin  
            q<=0;  
        end  
        else  
            begin  
                case({j,k})  
                    2'b00: q<=q;  
                    2'b01: q<=0;  

```

```

        2'b10: q<=1;
        2'b11: q<=qb;
    endcase
end
assign qb=~q;
end
endmodule

```

TESTBENCH:

```

module test;
    reg clk,rst,j,k;
    wire q,qb;
    tlsa a1(clk,rst,j,k,q,qb);
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
    end
    initial begin
        clk=0;
        forever #10 clk=~clk;
    end
    initial begin
        repeat(5) begin
            rst=$random;j=$random;k=$random;
            #10;
        end
    end

```

end

initial begin

 #60 \$finish();

end

endmodule

