

# PARITY CHECKER (EVEN OR ODD)

Now imagine a scenario. You want to send a stream of digital bits. Let's say that this stream has  $n$  bits. You are slightly concerned with errors entering your message. So you say, "Hey! I need to use some kind of error detection mechanism". So you decide to use 'parity bits.' Now you have two choices. You can either use the *even parity mechanism*. Or you can use the *odd parity mechanism*.



**Even parity mechanism:** The target is to make the total number of 1s even. For example, if you have a message signal "010", you can clearly see that it has just one 1. So we add a parity bit to make it two 1s. Now the number of 1s is even.

**Odd parity mechanism:** Here, the target is to make the total number of 1s odd. For example, consider the same message signal from above. "010". The parity bit here will


be....complete the sentence. *0!* That's right. There's already an odd number of 1s in the message signal.

## Parity Generator and Checker

### Even Parity Generator



### Odd Parity Checker

 

### RTL CODE:

```
module vl(input[7:0]a,output evenpar,output oddparr);  
    assign oddparr=~^(a);  
    assign evenpar=^(a);  
endmodule
```

### TESTBENCH:

```
module test;  
    reg [7:0] a;  
    wire evenpar,oddparr;  
    vl a1(a,evenpar,oddparr);  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);
```

```

end
initial begin
    repeat(5) begin
        a=$random;
        #10;
    end
end
end
initial begin
    #60 $finish();
end
endmodule

```

