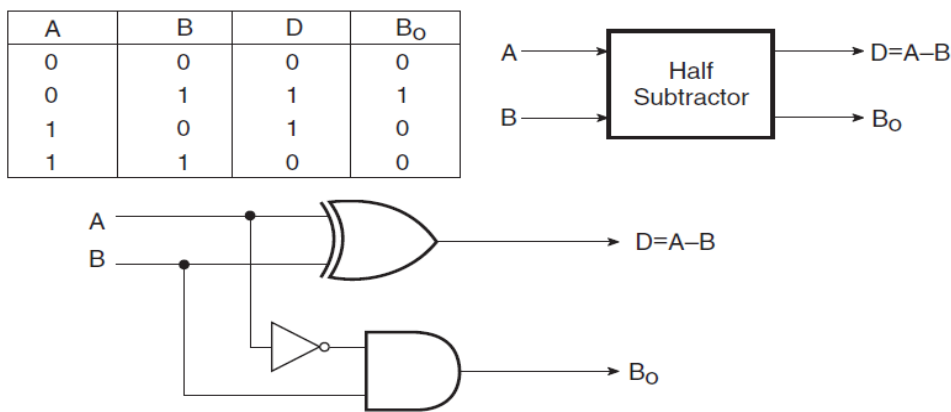


DAY-4

HALF SUBTRACTOR

EXPLANATION

Half subtractor is a combination circuit with two inputs and two outputs that are **different** and **borrow**. It produces the difference between the two binary bits at the input and also produces an output (Borrow) to indicate if a 1 has been borrowed. In the subtraction (A-B), A is called a **Minuend bit** and B is called a **Subtrahend bit**.



$$\text{Diff} = A'B + AB'$$

$$\text{Borrow} = A'B$$

APPLICATIONS:

1.Calculators: Most mini-computers utilize advanced rationale circuits to perform numerical tasks. A Half Subtractor can be utilized in a number cruncher to deduct two parallel digits from one another.

2.Alarm Frameworks: Many caution frameworks utilize computerized rationale circuits to identify and answer interlopers. A Half Subtractor can be utilized in these frameworks to look at the upsides of two parallel pieces and trigger a caution in the event that they are unique.

3.Automotive Frameworks: Numerous advanced vehicles utilize computerized rationale circuits to control different capabilities, like the motor administration framework, stopping mechanism, and theater setup. A Half Subtractor can be utilized in these frameworks to perform computations and examinations.

4.Security Frameworks: Advanced rationale circuits are usually utilized in security frameworks to identify and answer dangers. A Half Subtractor can be

utilized in these frameworks to look at two double qualities and trigger a caution in the event that they are unique.

RTL CODE:

BEHAVIOURAL METHOD:

```
module half_sub(d,b1,a,c);  
    output d,b1;  
    reg d,b1;  
    input a,c;  
    always@(a or c)  
    begin  
        d= a^c;  
        b1= (~a)&c;  
    end  
endmodule
```

DATA FLOW METHOD:

```
module half_sub(d,b1,a,c);  
    output d,b1;  
    input a,c;  
    assign d= a^c;  
    assign b1= (~a)&c;  
    end  
endmodule
```


STRUCTURAL METHOD:

```
module half_sub(d,b1,a,c);  
    output d,b1;  
    input a,c;  
    wire w1;  
    xor a1(d,a,c);  
    not b1(w1,a);  
    and c1(b,w1,c);  
endmodule
```

TEST BENCH:

```
module testbench;  
    reg a,c;  
    wire d,b1;  
    integer i;  
    half_sub a1(d,b1,a,c);  
    initial  
        begin  
            $dumpfile("dump.vcd");  
            $dumpvars(1);  
        end  
    initial  
        begin  
            a=0;c=0;  
        end  
    initial
```
 
```
begin
  for(i=1;i<4;i=i+1)
    begin
      #10 {a,c}=i;
    end
  end
end
initial
begin
  #60 $finish();
end
endmodule
```



Note: To revert to EPWave opening in a new browser window, set that option on your user page.