 


FULL SUBTRACTOR

EXPLANATION:

The Half Subtractor is used to subtract only two numbers. To overcome this problem, a full subtractor was designed. The full subtractor is used to subtract three 1-bit numbers A, B, and C, which are minuend, subtrahend, and borrow, respectively. The full subtractor has three input states and two output states i.e., diff and borrow.



DIFF: $(A \text{ XOR } B) \text{ XOR } B_{in}$

BORROW OUT: $A'B_{in} + A'B + BB_{in}$

APPLICATIONS:

Some of the **applications of full-subtractor** include the following

- These are generally employed for ALU (Arithmetic logic unit) in computers to subtract as CPU & GPU for the applications of graphics to decrease the circuit difficulty.
- Subtractors are mostly used for performing arithmetical functions like subtraction, in electronic calculators as well as digital devices.
- These are also applicable for different micro controllers for arithmetic subtraction, timers, and the program counter (PC)
- Subtractors are used in processors to compute tables, addresses, etc.
- It is also useful for DSP and networking based systems.
- These are used mainly for ALU within computers for subtracting like CPU & GPU for graphics applications to reduce the complexity of the circuit.
- These are mainly used to perform arithmetical functions such as subtraction within digital devices, calculators, etc.
- These subtractors are also appropriate for various microcontrollers for timers, PC (program counter) & arithmetic subtraction
- These are employed for processors to calculate addresses, tables, etc.
- The implementation of this with logic gates like NAND & NOR can be done with any full subtractor logic circuit because both the NOR & NAND gates are called universal gates.

RTL CODE:

DATA METHOD:

```
module full_sub(d,barr,a,b,c);  
    output d,barr;  
    input a,b,c;  
    assign d=a^b^c;  
    assign barr =(c& ~(a^b))|((~a)&b);  
endmodule
```

BEHAVIOURAL METHOD:

```
module full_sub(d,barr,a,b,c);  
    output reg d,barr;  
    input a,b,c;  
    always@(*)  
    begin  
        d=a^b^c;  
        barr =(c& ~(a^b))|((~a)&b);  
    end  
endmodule
```


TEST BENCH:

```
module testbench;  
    reg a,b,c;  
    wire d,barr;  
    integer i;  
    full_sub a1(d,barr,a,b,c);  
    initial  
    begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
    end  
    initial  
    begin  
        a=0;b=0;c=0;
```


```

end
initial
begin
    for(i=1;i<8;i=i+1)
        begin
            #10 {a,b,c}=i;
        end
    end
end
initial
begin
    #60 $finish();
end
endmodule

```

 

FULLSUBTRACTOR USING HALF SUBTRACTOR

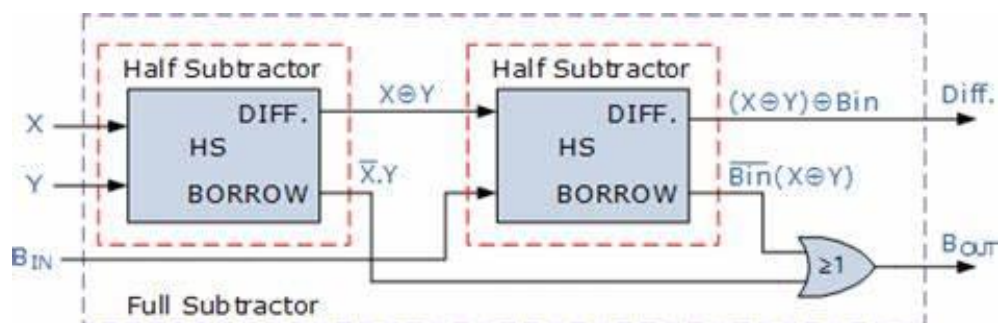

RTL CODE:

```

module full_subtractor(d,barr,a,b,c);

input a,b,c;

output d,barr;

```

```
wire p, q, r;

half_subtractor u4(p,q,a,b);

half_subtractor u5(d,p,c);

or_gate u6(barr, p,q);

endmodule
```

TEST BENCH:

```
module testbench;

    reg a,b,c;

    wire d,barr;

    integer i;

    full_sub a1(d,barr,a,b,c);

    initial

        begin

            $dumpfile("dump.vcd");

            $dumpvars(1);

        end

    initial

        begin

            a=0;b=0;c=0;

        end

    initial

        begin

            for(i=1;i<8;i=i+1)

                begin
```

```
        #10 {a,b,c}=i;  
    end  
end  
initial  
begin  
    #60 $finish();  
end  
endmodule
```