 


2:4 DECODER

A [decoder](#) is a combinational logic circuit that has 'n' input signal lines and 2^n output lines. In the 2:4 decoder, we have 2 input lines and 4 output lines. In addition, we provide 'enable' to the input to ensure the decoder is functioning whenever enable is 1 and it is turned off when enable is 0. The truth table, logic diagram, and logic symbol are given below:



| X | Y | F0 | F1 | F2 | F3 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

RTL CODE:

```
module tal(input en,input [1:0]a,output reg [3:0]y);
```

```
  always @(*)
```

```
  begin
```

```
    if(en)begin
```

```
      case(a)
```

```

        2'b00: y=4'b0001;
        2'b01: y=4'b0010;
        2'b10: y=4'b0100;
        2'b11: y=4'b1000;
    endcase
end
else
    y=4'b1111;
end
endmodule

```


TESTBENCH:

```

module test;
    reg en;
    reg [1:0]a;
    wire [3:0]y;
    tal t1(en,a,y);
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(1);
    end
    initial begin
        a=2'b00;en=0;
        #10 a=2'b00;en=1;
        #10 a=2'b01;en=1;
        #10 a=2'b10;en=1;
    end
endmodule

```
 
```
#10 a=2'b11;en=1;
end
initial begin
    #60 $finish();
end
endmodule
```



Note: To revert to EPWave opening in a new browser window, set that option on your user page.