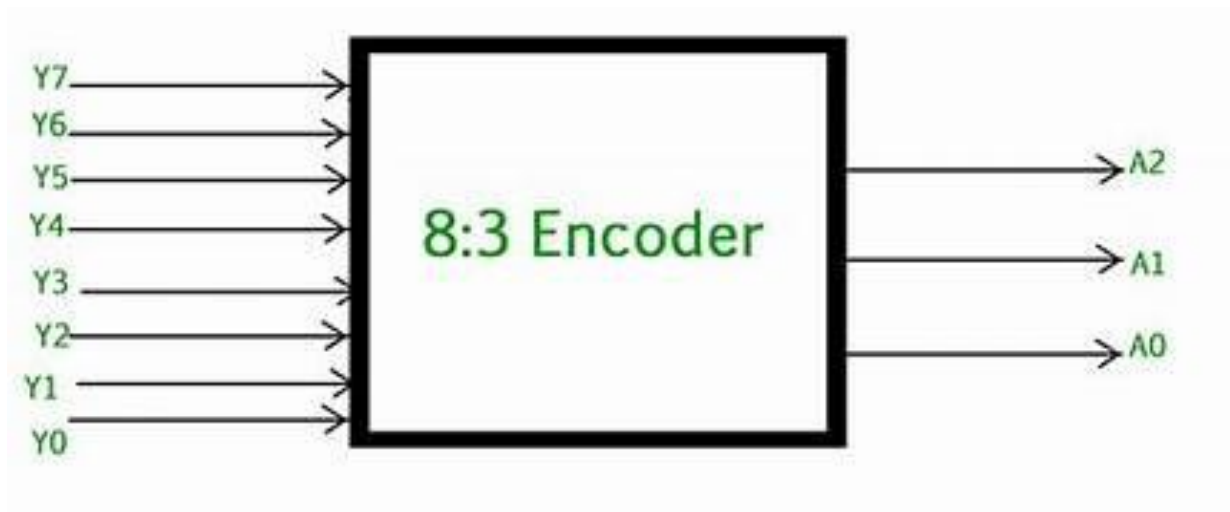


8:3 ENCODER

The 8 to 3 line Encoder is also known as **Octal to Binary Encoder**. In 8 to 3 line encoder, there is a total of eight inputs, i.e., $Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6,$ and Y_7 and three outputs, i.e., $A_0, A_1,$ and A_2 . In 8-input lines, one input-line is set to true at a time to get the respective binary code in the output side. Below are the block diagram and the truth table of the 8 to 3 line encoder



RTL CODE:

```
module binary_encoder(  
    input [7:0] D,  
    output [2:0] y);  
  
    assign y[2] = D[4] | D[5] | D[6] | D[7];  
    assign y[1] = D[2] | D[3] | D[6] | D[7];  
    assign y[0] = D[1] | D[3] | D[5] | D[7];  
endmodule
```

```
endmodule
```

TESTBENCH:

```
module tb;
```

```
    reg [7:0] D;
```

```
    wire [2:0] y;
```

```
    int i;
```

```
    binary_encoder bin_enc(D, y);
```

```
    initial begin
```

```
        $dumpfile("dump.vcd");
```

```
        $dumpvars(1);
```

```
    end
```

```
    initial begin
```

```
        D=8'b1;
```

```
        for(i=0; i<8; i++) begin
```

```
            #10 D=D<<1;
```

```
        end
```


```
    end
```

```
    initial begin
```

```
        #60 $finish();
```

```
    end
```

```
endmodule
```

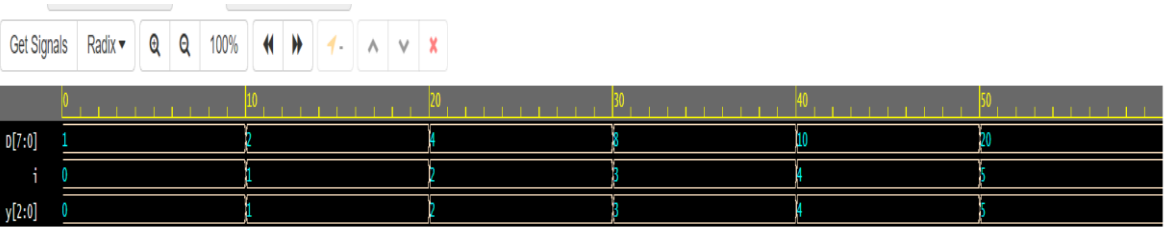

Note: To revert to FPGAWave in a new browser window, set that option on your user name.