 


2 x 1 MUX

In 2×1 multiplexer, there are only two inputs, i.e., A_0 and A_1 , 1 selection line, i.e., S_0 and single outputs, i.e., Y . On the basis of the combination of inputs which are present at the selection line S^0 , one of these 2 inputs will be connected to the output. The block diagram and the truth table of the 2×1 multiplexer are given below.



RTL CODE:

```
module mux(input i0,input i1,input s,output y);  
    assign y=s?i1:i0;  
endmodule
```


TESTBENCH

```
module test;  
    reg i0,i1,s;  
    wire y;  
    mux a1(i0,i1,s,y);  
    initial begin
```

```

    $dumpfile("dump.vcd");
    $dumpvars(1);
end
initial begin
    i0=1'b1;i1=1'b0;s=1'b0;
    #10 i0=1'b0;i1=1'b1;s=1'b1;
end
initial begin
    #10 $finish();
end
endmodule


```

 

Note: To revert to EPIWave opening in a new browser window, set that option on your user page.

4X1 MUX

 4x1 Multiplexer has four data inputs I_3 , I_2 , I_1 & I_0 , two selection lines s_1 & s_0 and one output Y. The **block diagram** of 4x1 Multiplexer is shown in the following figure.



RTL CODE:

```

module mux(input [3:0]i,input[1:0]s,output reg y);
    always @( * )
    begin
        case(s)
            2'b00: y=i[0];
            2'b01: y=i[1];
            2'b10: y=i[2];
            2'b11: y=i[3];
        endcase
    end
endmodule

```

TESTBENCH:

```

module test;
    reg [3:0]i;
    reg [1:0]s;
    wire y;
    mux a1(i,s,y);

```

```

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
end

initial begin
    s[0]=1'b0;s[1]=1'b0;i[0]=1'b1;i[1]=1'b0;i[2]=1'b0;i[3]=1'b0;
    #10 s[0]=1'b0;s[1]=1'b1;i[0]=1'b0;i[1]=1'b1;i[2]=1'b0;i[3]=1'b0;
    #10 s[0]=1'b1;s[1]=1'b0;i[0]=1'b0;i[1]=1'b0;i[2]=1'b1;i[3]=1'b0;
    #10 s[0]=1'b1;s[1]=1'b1;i[0]=1'b0;i[1]=1'b0;i[2]=1'b0;i[3]=1'b1;
end

initial begin
    #60 $finish();
end

endmodule

```



Note: To revert to EPIWave opening in a new browser window, set that option on your user page.